

Week 3 Tutorial

Question 1. Consider a linear continuous-time system described by the equations

$$\begin{aligned}\dot{x}_1(t) &= x_1(t) + \alpha x_2 + u(t) \\ \dot{x}_2(t) &= x_1(t) + x_2(t) - \alpha x_2(t) \\ y(t) &= x_1(t)\end{aligned}$$

with $\alpha \in \mathbb{R}$ and constant, $x(t) = [x_1(t), x_2(t)]^T \in \mathbb{R}^2$ and $u(t) \in \mathbb{R}$.

1. Let $u(t) = 0$, for all $t \geq 0$. Compute the equilibrium points of the system as a function of α .
2. Assume now $u(t) = u(0)$, for all $t \geq 0$, where $u(t) \neq 0$. Compute the equilibrium points of the system as a function of α .
3. Discuss similarities and differences between the results in part (a) and part (b).

Question 2. An ideal op-amp circuit is given in Figure 1

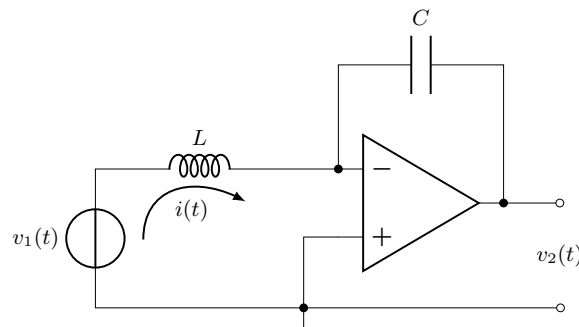


Figure 1

where $i(t)$ is the current, $v_1(t)$ is the input and $v_2(t)$ is the output.

1. Derive the state space model for the circuit in Figure 1 using the state variables $x_1 = i(t)$ and $x_2 = v_2(t)$.
2. Using your answer from part 1, obtain the transfer function $G(s)$ of the circuit in Figure 1.
3. Find the state transition matrix e^{At} such that $\mathbf{x}(t) = e^{At}\mathbf{x}(0)$.
4. Find the equilibrium point of the circuit in Figure 1.